

# Examination cover sheet

(to be completed by the examiner)

Course name: Sensing, Computing, Actuating

Course code: 5AIB0

Date: 9-8-2016

Start time: 13:30

End time : 16:30

Number of pages: 8

Number of questions: 3

Maximum number of points/distribution of points over questions: 90

Method of determining final grade: divide total of points by 9

Answering style: open questions

Exam inspection: make appointment via email with the responsible lecturer

Other remarks:

## Instructions for students and invigilators

Permitted examination aids (to be supplied by students):

- Notebook
- Calculator
- Graphic calculator
- Lecture notes/book
- One A4 sheet of annotations
- Dictionar(y)(ies). If yes, please specify:
- Other:

### Important:

- examinees are only permitted to visit the toilets under supervision
- it is not permitted to leave the examination room within 15 minutes of the start and within the final 15 minutes of the examination, unless stated otherwise
- examination scripts (fully completed examination paper, stating name, student number, etc.) must always be handed in
- the house rules must be observed during the examination
- the instructions of examiners and invigilators must be followed
- no pencil cases are permitted on desks
- examinees are not permitted to share examination aids or lend them to each other

During written examinations, the following actions will **in any case** be deemed to constitute fraud or attempted fraud:

- using another person's proof of identity/campus card (student identity card)
- having a mobile telephone or any other type of media-carrying device on your desk or in your clothes
- using, or attempting to use, unauthorized resources and aids, such as the internet, a mobile telephone, etc.
- using a clicker that does not belong to you
- having any paper at hand other than that provided by TU/e, unless stated otherwise
- visiting the toilet (or going outside) without permission or supervision

Final Exam  
5AIB0 Sensing, Computing, Actuating  
9-8-2016, 13:30-16:30

- This final exam consists of 3 questions for which you can score at most 90 points. The final grade for this exam is determined by dividing the number of points you scored by 9.
- The solutions to the exercises should be clearly formulated and written down properly. Do not only provide the final answer. Explain your choices and show the results of intermediate steps in your computation.
- The use of a simple calculator is allowed. No graphical calculator or laptop may be used during the exam.

## Formulae sheet

Characteristic temperature of material:  $B_{T_1/T_2} = \frac{\ln\left(\frac{R_2}{R_1}\right)}{\frac{1}{T_1} - \frac{1}{T_2}}$

Resistance:  $R = \frac{m}{ne^2\tau} \frac{l}{A} = \rho \frac{l}{A}$

Strain:  $\epsilon = \frac{dl}{l}$

Stress:  $\sigma = \frac{F}{A} = E \frac{dl}{l}$

Poisson's ratio:  $\nu = -\frac{dt/t}{dl/l}$

Change in specific resistance due to volume change (for metals):  $\frac{d\rho}{\rho} = C \frac{dV}{V}$

Change in resistance due to strain:  $\frac{dR}{R} = G\epsilon$

Capacitance of flat plate capacitor:  $C = \frac{q}{V} = \epsilon_0 \epsilon_r \frac{A}{d}$

Capacitance of cylindrical capacitor:  $C = \frac{q}{V} = \epsilon_0 \epsilon_r \frac{2\pi \cdot l}{\ln(b/a)}$

Energy stored in capacitor:  $E = \frac{C \cdot V^2}{2}$

Reluctance:  $\mathfrak{R} = \frac{1}{\mu\mu_0} \frac{l}{A}$

Inductance:  $L = \frac{N \cdot \Phi}{i} = \frac{N^2}{\mathfrak{R}}$

Flux:  $\Phi = \mathbf{B} \times \mathbf{S}$

Magneto-motive force:  $F_m = \Phi \cdot \mathfrak{R} = N \cdot i$

Amplitude response of Butterworth LPF:  $|H(f)| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_n}\right)^{2n}}}$

Sideways force on electron moving through magnetic field:  $\mathbf{F} = q \cdot \mathbf{v} \times \mathbf{B}$

Transverse Hall potential:  $V_H = \frac{1}{N \cdot c \cdot q} \frac{i \cdot B}{d} \sin(\alpha)$

Radius of warping of bimetal sensor:  $r \approx \frac{2j}{3(\alpha_x - \alpha_y)(T_2 - T_1)}$

Displacement of bimetal sensor:  $\Delta = r(1 - \cos(\frac{180L}{\pi r}))$

Flow velocity and temperature difference:  $v = \frac{K}{\rho} \left( \frac{e^2}{R_S} \frac{1}{T_s - T_0} \right)^{1.87}$

Voltage across P-N junction (quality factor 1):  $V = \frac{kT}{q} \ln\left(\frac{I}{I_0}\right)$

Saturation current through PN-junction (quality factor 1):  $I_0 = BT^3 e^{-E_g/kT}$

Thomson effect:  $Q = I^2 \cdot R - I \cdot \sigma \frac{dT}{dx}$

Peltier coefficient:  $\pi_{AB}(T) = T \cdot (\alpha_A - \alpha_B) = -\pi_{BA}(T)$

**Exercise 1: exhaust gas temperature measurement****(30 points)**

It is necessary to change the ratio between fuel and air in a combustion engine to maximize the efficiency of the engine. The objective is to keep the temperature of the gasses going through the exhaust pipe within a certain temperature range. Because of the high temperature of these gases, it is necessary to use a thermocouple to measure this temperature. A thermocouple can only measure a temperature difference. Therefore it is necessary to also add a reference sensor to the circuit. This sensor is then used to measure the absolute temperature at the reference junction.

The thermocouple in Figure 1 contains a reference junction compensation based on a RTD temperature sensor. The output voltage of this sensor ( $v_{ref}$ ) is given by the following transfer function:  $v_{ref} = 10mV/^{\circ}C \cdot T_a$  with  $T_a$  the environmental temperature at the reference junction. The output of the reference temperature sensor is connected to the reference input of the instrumentation amplifier. It holds for this instrumentation amplifier:

$$v_o - v_{ref} = \left(1 + \frac{2R_2}{R_1}\right) \frac{R_4}{R_3} (v_2 - v_1) = (1 + G) k (v_2 - v_1)$$

The ratio of the resistors in the instrumentation amplifier is equal to:  $k = R_4/R_3 = 1$ . The thermocouple itself is a J-type (Cn/Fe) thermocouple with a sensitivity  $S_J = 54\mu V/K$ .

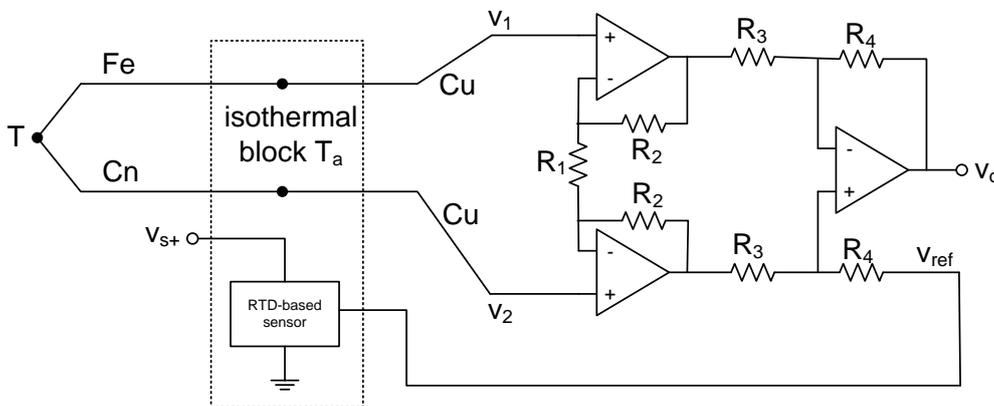


Figure 1: Compensation with a RTD-based sensor and instrumentation amplifier.

- (5p) (a) There are three important laws that you can use when analysing thermocouples, namely the law of the homogeneous circuits, the law of intermediate metals, and the law of intermediate temperatures. Show using these laws that the voltage across the thermocouple shown in Figure 1 is equal to:

$$v_2 - v_1 = V_T - V_{T_a} = S_J \cdot (T - T_a)$$

*Hint:* The Seebeck coefficient  $\alpha_{Cn/Fe}$  of a J-type thermocouple is equal to:  $\alpha_{Cn/Fe} = S_J$ .

- (5p) (b) What gain,  $G$ , should the instrumentation amplifier have to get an output voltage  $v_o$  that is independent of the environmental temperature?

Exercise continues on next page

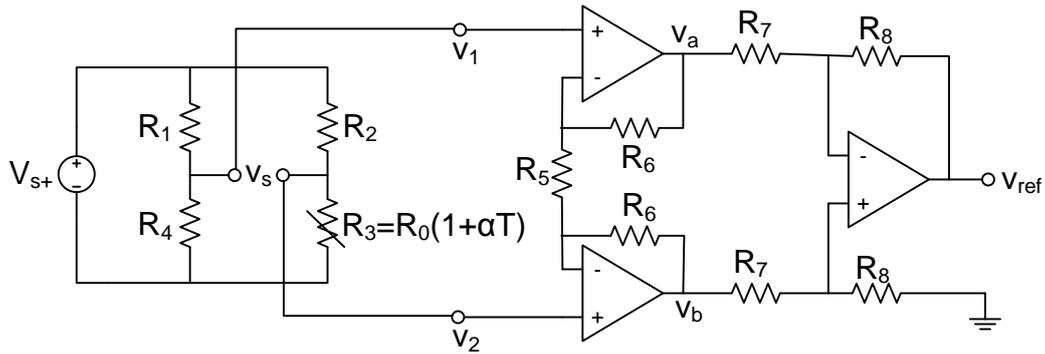


Figure 2: Implementation of “RTD-based sensor” block of Figure 1.

- (5p) (c) The circuit shown in Figure 2 is used to generate the reference voltage  $v_{ref}$  for the thermocouple sensor shown in Figure 1. In other words, Figure 2 shows the internals of the block “RTD-based sensor” in Figure 1. Assume that the supply voltage  $v_{s+}$  is equal to 5 V. Assume further that resistor  $R_3$  is a temperature dependent resistor (RTD) of type PT100. Its relation between temperature and resistance (transfer function) can be approximated with the following linear equation:  $R_3(T) = R_0(1 + \alpha T)$ , with  $R_0$  equal to  $100\Omega$  and  $\alpha = 0.004/^\circ C$ . Assume also that  $R_4 = R_5 = R_6 = R_7 = R_8 = R_0$  and  $R_1 = R_2 = k \cdot R_0$ . What resistance should the resistor  $R_2$  have to ensure that the “RTD-based sensor” has a sensitivity of  $10mV/^\circ C$ ?
- (5p) (d) The operation of a temperature dependent resistor (RTD) is based on the thermo-resistive effect. Explain briefly (maximal 200 words) how this effect works in metals.

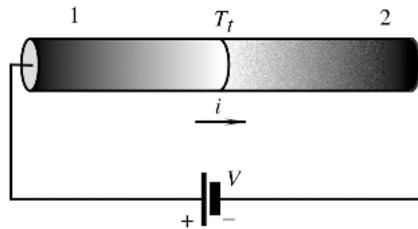


Figure 3: Peltier effect in single junction.

- (5p) (e) Figure 3 shows a single junction of two different materials. Explain (in maximally 200 words) why the Peltier effect results in the production or liberation of energy at a junction when a current is passed through this junction.
- (5p) (f) Give at least three reasons why we prefer transducers who produce a signal in the electrical domain over transducers that produce a signal in any of the other signal domains.

**Exercise 2: inductive sensor**

**(30 points)**

Figure 4 shows a two coil based linear displacement transformer that can be used to sense the displacement of an object over a distance  $x$ . The two coils each consist of  $N$  windings and are connected in series to each other. An excitation voltage  $v_e$  is placed over the two coils. The voltage drop over one of the coil (i.e., lower coil in Figure 4) is used as the output voltage  $v_o$  of the sensor.

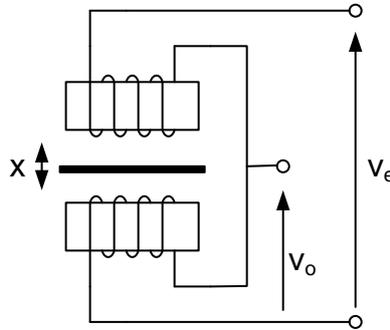


Figure 4: Inductive sensor based on two coils in series.

(5p) (a) Show that the output voltage of the sensor is equal to:

$$v_o = \frac{1 - x}{2} v_e$$

(3p) (b) Is this sensor suitable to measure large displacements? (Explain your answer)

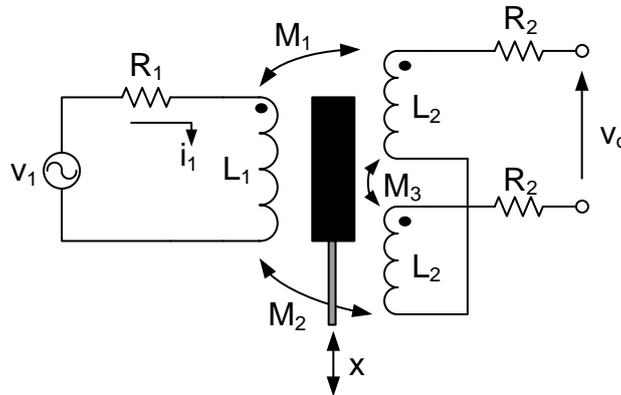


Figure 5: LVDT sensor.

(4p) (c) The linear variable differential transducer (LVDT) shown in Figure 5 is often used to sense displacements instead of the two coil sensor shown in Figure 4. When a purely resistive load  $R_L$  is connected to the output of the sensor, its output voltage is equal to:

$$V_o = \frac{j\omega k_x x R_L}{-(j\omega)^2 2L_1 L_2 - j\omega(R_{2c} L_1 + 2R_1 L_2) - R_1 R_{2c}} V_1$$

, with  $R_{2c} = 2R_2 + R_L$ . For a specific LVDT holds that its primary winding has a DC resistance of  $76 \Omega$  and each of its two secondary windings have individually a DC resistance of  $1600 \Omega$ . The primary winding has an inductance of  $45 \text{ mH}$  and the two secondary windings have a combined inductance of  $366 \text{ mH}$ . How large is the phase shift between the input and output voltage when an excitation frequency of  $1500 \text{ Hz}$  is used and a load resistance of  $10 \text{ k}\Omega$  is connected to the output of the sensor?

**Exercise continues on next page**

- (5p) (d) The phase shift that you computed in the previous question can be reduced by increasing the load resistance. How large should the load resistance  $R_L$  be to ensure that there is no phase shift between the input and output voltage of the sensor when an input voltage with an excitation frequency of  $1500 \text{ Hz}$  is used?

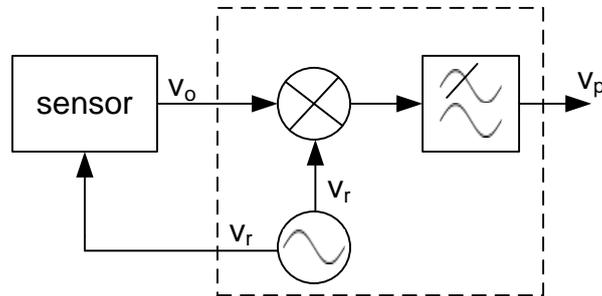


Figure 6: Sensor with phase sensitive detector.

- (5p) (e) The displacement sensor from Figure 5 is connected to a phase sensitive detector. This detector consists of an analog multiplier connected to a low-pass filter. Using this processing circuit, it is possible to recover the magnitude and direction of the displacement from the output signal of the sensor. The block diagram of a phase sensitive detector is shown in Figure 6. The displacement of the object is given as a function  $x(t)$ . Assume further that the reference voltage  $v_r$  is equal to:

$$v_r(t) = V_r \cos(\omega_r \cdot t)$$

The output voltage  $v_o$  of the sensor circuit is then equal to:

$$v_o(t) = S \cdot x(t) \cdot v_r(t)$$

, with  $S$  the sensitivity of the sensor.

Show that the output voltage of the phase sensitive detector,  $v_p$ , is equal to:

$$v_p(t) = S \cdot x(t) \cdot \frac{V_r^2}{2}$$

*Hint:*  $\cos(A)\cos(B) = \frac{1}{2}(\cos(A+B) + \cos(A-B))$ .

- (4p) (f) The output of the phase sensitive detector can be connected to an AD converter. Alternatively the output of the sensor could immediately be connected to an AD converter. Give at least one reason why we prefer to use a phase sensitive detector in front of the AD converter instead of directly connecting the output of the sensor to the AD converter.
- (4p) (g) A LVDT measures the displacement of an object through the change in coupling between a primary and two secondary coils. Another way to measure a displacement would be to use a Hall effect sensor. Explain the operation of a Hall effect sensor. Clearly indicate how you can use the sensor to measure a displacement.

**Exercise 3: throttle position sensor****(30 points)**

The driver of a car can control the power delivered by the engine through the throttle pedal. When moving this pedal, the driver changes the amount of fuel or the fuel/air mixture. This allows the driver to control the speed of the car. Traditionally, the throttle pedal has been connected with a carburetor valve using a so called bowden cable. Modern cars use a “drive-by-wire” system that replaces this cable with an electric system. These systems use a sensor to sense the position of the throttle pedal. One option would be to use a resistive displacement sensor such as the one shown in Figure 7. This sensor can be used to measure linear displacements of an object. The sensor consists of a variable resistor  $R_T$ , a fixed resistor  $R_s = R_T/a = 3000 \Omega$  and a constant voltage supply  $V_r = 9 \text{ V}$ . The sensor is connected to a measurement circuit with a purely resistive impedance  $R_m = R_T/b$  with a resistance of  $3000 \Omega$  (i.e.,  $a = b$ ). This measurement load causes a loading error in the output voltage  $v_m$  of the sensor.

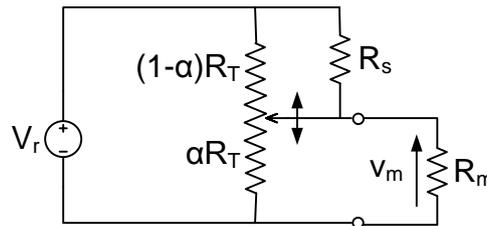


Figure 7: Displacementsensor with processing circuit.

- (5p) (a) Show that the output voltage  $v_m$  of the circuit shown in Figure 7 is equal to:

$$v_m = \frac{\alpha(1+a(1-\alpha))}{1+\alpha(1-\alpha)(a+b)} V_r$$

- (5p) (b) Show that the relative error in the output voltage of the sensor due to the loading circuit  $R_m$  is equal to:

$$\epsilon = \left| \frac{\alpha(1-\alpha)b}{1+\alpha(1-\alpha)(a+b)} \right|$$

- (5p) (c) A certain application requires that the relative error of the sensor at  $\alpha = 0.75$  is not more than 3%. What value should the resistor  $R_T$  to ensure that this constraint is met?
- (2p) (d) Instead of using a resistive displacement sensor, you could also use an inductive displacement sensor. Give at least one advantage of using an inductive displacement sensor over a resistive displacement sensor.

Exercise continues on next page

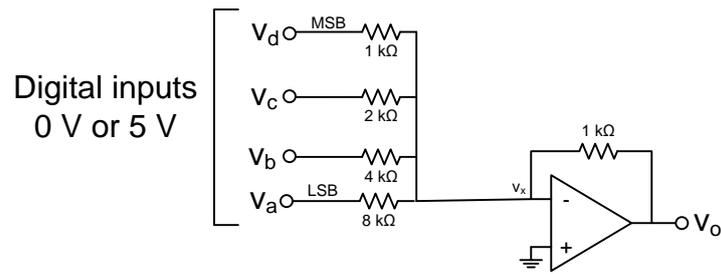


Figure 8: DA converter using summing op-amp.

- (5p) (e) A summing DA converter is shown in Figure 8. Which binary input has been applied to the DA converter if it has an output voltage  $v_o$  of 1.9V?
- (8p) (f) Give a definition (maximally 100 words) for the following terms:
- Transducer
  - Sensor
  - Sensitivity of a sensor
  - Transfer function of a sensor