

Sensing, Computing, Actuating

Lecture 14 - Thermocouple

Exercise 1: Gasoline exhaust gas temperature measurement

To maximize the fuel efficiency of a gasoline engine and to minimize the toxic gases exhausted by the engine, the engine control unit will regulate the fuel/air mixture to keep the temperature of the exhaust gas within certain limits. Exhaust gases in a gasoline engine are lower than in a diesel engine, but they may still reach temperatures between 700°C and 1200°C . A K-type thermocouple can be used to measure the temperature of this gas. Figure 1 shows a circuit to measure a temperature T by means of such a K-type thermocouple. The ambient temperature T_a at the reference junction is compensated using a NTC thermistor. The thermocouple has a sensitivity $k = 41 \mu\text{V}/\text{K}$. The NTC thermistor has $B = 3546 \text{ K}$ and resistance $R_0 = 10 \text{ k}\Omega$ at 25°C . The voltage source $V_R = 1.35 \text{ V}$ and $R_2 = 100 \Omega$. The output voltage of the circuit $v_o = k \cdot T$ (with T in $^{\circ}\text{C}$).

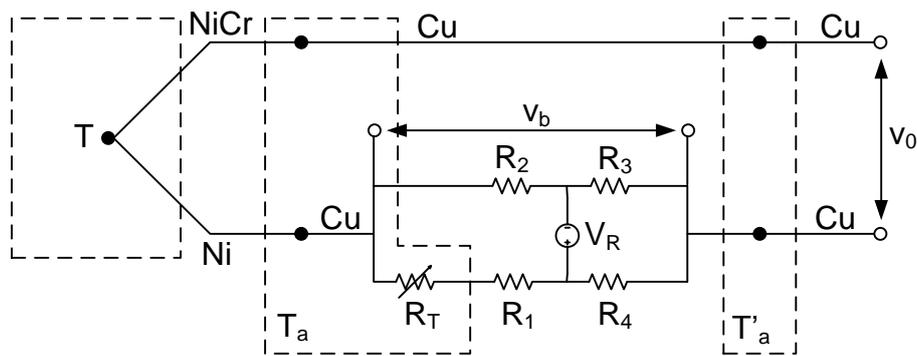


Figure 1: Circuit for cold junction compensation.

- Draw an equivalent circuit that represents the three thermocouple junctions and the bridge as voltage sources. (Note your circuit should contain in total four voltage sources, i.e., V_T , $V(\text{NiCr}/\text{Cu})$, $V(\text{Ni}/\text{Cu})$, and V_b .)
- Show that the bridge output voltage V_b should be equal to $k \cdot T_a$ to compensate for the ambient temperature T_a . (Hint: use law of intermediate metals.)
- Show that the bridge sensitivity at the reference junction is equal to:

$$\frac{dV_b}{dT} = \left(\frac{\frac{BR_2}{T^2} R_0 e^{B(1/T-1/T_0)}}{(R_1 + R_0 e^{B(1/T-1/T_0)} + R_2)^2} \right) V_R$$

- In question 1(b), you showed that the output voltage V_b should be equal to $k \cdot T_a$ to compensate for the ambient temperature T_a . Hence, the bridge should have a sensitivity k . What value for R_1 should be used to ensure that the bridge sensitivity is equal to k ?
- What ratio should R_3/R_4 have to ensure that the circuit shown in Figure 1 compensates the ambient temperature at the reference junction?